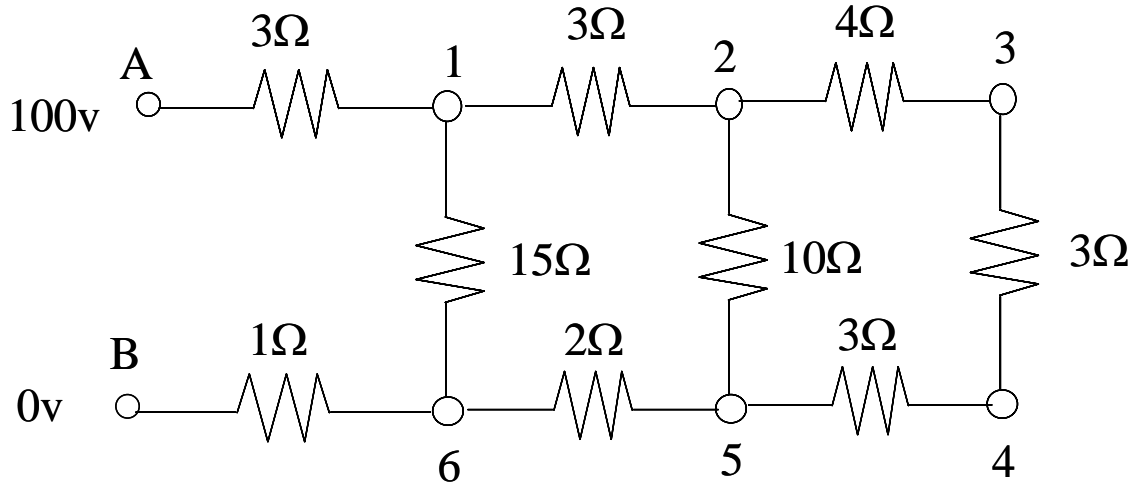


ME 534 COMPUTER-BASED MODELING AND SIMULATION
Instructor: Prof. Cagatay Basdogan



The Ohm's Law states that, I_{pq} , the current flowing from node p to node q in leg pq of an electrical network, is given by

$$I_{pq} = \frac{v_p - v_q}{R_{pq}}$$

where v_p and v_q are the voltages at nodes p and q , respectively, and R_{pq} is the resistance of leg pq . In addition, the Kirchoff's Current Law states that the sum of the currents arriving at each node must be zero. For example, the application of these laws at node 1 in the electrical network shown above leads to

$$I_{A1} + I_{21} + I_{61} = \frac{100 - v_1}{3} + \frac{v_2 - v_1}{3} + \frac{v_6 - v_1}{15} = 0$$

or

$$11v_1 - 5v_2 - v_6 = 500$$

- (a) Derive the linear equations whose solutions are the potentials at nodes 1 through 6 in the electrical network shown above.
- (b) Write a C/C++ program to calculate the voltages at the nodes using the LU decomposition method discussed in "Numerical Recipes".